

EE 172 – UNIT 2

DC Machines

Short Detailed Notes

2.1 INTRODUCTION

What is a DC Machine?

- Essentially an **AC machine** with a **commutator**
- The commutator **converts AC to DC** (or DC to AC)
- Can operate as either a **motor** or **generator**

Classification of DC Machines

Separately Excited	Self-Excited
Field winding connected to external source	Field winding powered by its own armature
More expensive	More common
Quicker response to control	Three types: Shunt, Series, Compound

Self-Excited Types

- 1 **Shunt Machine** – Field winding in **parallel** with armature
- 2 **Series Machine** – Field winding in **series** with armature
- 3 **Compound Machine** – Combination of shunt and series (not covered)

2.2 SEPARATELY EXCITED MACHINES

Key Feature

- Field winding gets power from an **independent external source**
- Armature and field circuits are **electrically separate**

Applications

- Where **precise control** is needed
- Laboratory/research experiments
- Quick response to field changes

2.3 SELF-EXCITED MACHINES

Key Feature

- Field winding gets power from the **machine's own armature**
- Three types: **Shunt, Series, Compound**
- Different modes of connecting field coils to armature

2.4 DC GENERATORS

Constructional Features

Main Parts:

- 1 **Field Yoke** – Carries magnetic flux, provides mechanical support
- 2 **Pole Cores** – Support field windings
- 3 **Air Gap** – Between poles and armature
- 4 **Armature Core** – Rotating part with windings
- 5 **Commutator** – Converts AC to DC
- 6 **Brushes** – Collect current from commutator

Additional Features:

- **Interpoles (Commutating Poles)** – Placed midway between main poles
- Purpose: **Improve commutation**
- Active only when armature current flows

Magnetic Circuit: Field yoke → pole cores → air gap → armature core

Electric Circuits: Armature winding, commutator, brushes, field windings

2.4.1 Voltage Equation of DC Generator

Definitions:

Symbol	Meaning
P	Number of poles
Φ	Useful flux per pole (Webers)
Z	Total conductors on armature
N	Speed (rpm)
b	Number of parallel paths in armature
E_g	Generated emf

Formula:

$$E_g = (P \times \Phi \times Z \times N) / (60 \times b)$$

For Different Windings:

Lap Winding	Wave Winding
$b = P$	$b = 2$
Used for high current	Used for high voltage

Simplified Form:

$$E_g = K_1 \times \Phi \times N$$

where $K_1 = PZ/(60b)$ (constant for a machine)

Example 1 – Generator Voltage Calculation

Problem: 60kW, 4-pole generator, lap winding, 48 slots $\times$ 6 conductors/slot, $\Phi = 0.08$ Wb, $N = 1040$ rpm

$$Z = 48 \times 6 = 288 \text{ conductors}$$

$$b = P = 4 \text{ (lap winding)}$$

$$E_g = (4 \times 0.08 \times 288 \times 1040) / (60 \times 4)$$

$$E_g = 400 \text{ V}$$

$$\text{Load Current: } I = P/V = 60,000/400 = 150 \text{ A}$$

$$\text{Conductor current} = 150/4 = 37.5 \text{ A (4 parallel paths)}$$

2.4.2 Armature Reaction in Generators

Definition: The distorting effect of armature current flux on the main field flux

Causes:

- When armature delivers current, it produces its own magnetic field
- This field **interacts** with the main field

Two Main Effects:

- 1 **Demagnetizing** – Weakens main flux $\rightarrow$ reduces voltage
- 2 **Cross-magnetizing** – Distorts flux distribution $\rightarrow$ causes sparking at brushes

2.4.3 Compensating Windings

Purpose: Neutralize cross-magnetizing effect

Construction:

- Embedded in **pole faces**
- Connected in **series** with armature
- Carry **same current** as armature

Applications:

- High speed DC machines
- High voltage DC machines
- Large capacity machines

- Machines subject to large load fluctuations

2.4.4 Load Characteristics of DC Generators

Three Important Characteristics:

Characteristic	Shows Relationship
No-Load Saturation (OCC)	E_o vs I_f (generated emf vs field current)
Internal Characteristic	E vs I_a (generated emf vs armature current)
External (Load) Characteristic	V vs I (terminal voltage vs load current)

2.4.4.1 No-Load Characteristics (Separately Excited)

- Also called **Open-Circuit Characteristic (OCC)**
- Shows relationship between **no-load generated emf** and **field current**
- Taken at **constant speed**

2.4.4.2 Load Characteristics (Separately Excited)

- Also called **Voltage Regulation Curve**
- Shows relationship between **terminal voltage** and **load current**

Why Terminal Voltage Drops Under Load:

- 1 **Armature reaction** – Distorts/weakens main flux
- 2 **IR drop** – Resistance of armature and brushes

Terminal Voltage Equation:

$$V = E_g - I_a \times R_a$$

Example 2 – Voltage Change with Speed and Field

Problem: $E_g = 200V$ at $N=1200$ rpm, $I_f=2.5A$

(a) At $N=1600$ rpm, $I_f=2.5A$:

$$E_{g2} = E_{g1} \times (N_2/N_1) \times (I_{f2}/I_{f1})$$

$$E_{g2} = 200 \times (1600/1200) \times (2.5/2.5) = 266.67 \text{ V}$$

(b) At $N=1000$ rpm, $I_f=3.0A$:

$$E_{g2} = 200 \times (1000/1200) \times (3.0/2.5) = 200 \text{ V}$$

Key Formula:

$$E_g \propto I_f \times N$$

2.4.5 Applications of Separately Excited Generators

- **More expensive** than self-excited
- Used when **quick response** is needed

- **Precise control** of output
- **Laboratory/research** applications

2.4.6 Shunt Generators

Connection: Field winding in **parallel** with armature

Key Equations:

$$I_{sh} = V / R_{sh} \text{ (Field current)}$$

$$I_a = I_{sh} + I \text{ (Armature current)}$$

$$V = E_g - I_a \times R_a \text{ (Terminal voltage)}$$

$$\text{Power Developed} = E_g \times I_a$$

$$\text{Power Delivered} = V \times I$$

Factors for Voltage Drop:

- 1 **Armature reaction** – weakens flux
- 2 **Armature resistance drop** – $I_a R_a$ loss
- 3 **Reduction in field current** – lower voltage means lower field current

Characteristics:

- **Fairly constant** output voltage
- Rated as **constant voltage** generator

Applications:

- Supplying excitation to AC generators
- Short distance applications
- **Charging storage batteries**

Example 3 – Shunt Generator Calculations

Problem: Delivers 96A at 240V, $R_a = 0.15\Omega$, $R_f = 60\Omega$, brush drop = 2V

(a) Field current: $I_f = 240/60 = 4A$
 Armature current: $I_a = I_f + I_L = 4 + 96 = 100A$

(b) Generated voltage:
 $E_g = V_t + I_a R_a + V_{brush}$
 $E_g = 240 + (100 \times 0.15) + 2 = 257V$

2.4.7 Series Generators

Connection: Armature, field, and load all in **series**

Key Equations:

$$I_a = I_{se} = I \text{ (Same current everywhere)}$$

$$V = E_g - I(R_a + R_{se}) \text{ (Terminal voltage)}$$

$$\text{Power Developed} = E_g \times I$$

$$\text{Power Delivered} = V \times I$$

Characteristics:

- **Rising voltage** with load initially
- Voltage increases until **saturation**
- **Unstable** characteristic

Why Curve is Lower than Saturation Curve:

- 1 Armature reaction reduces flux
- 2 Resistance drops in armature, field, and brushes

Applications:

- **Voltage boosting** (where voltage needs to increase with current)
- Supplying field current for **regenerative braking** of DC locomotives

Limitation: Unstable characteristic limits general use

2.5 DC MOTORS

Classification

- 1 **DC Motors** – Run on DC supply
- 2 **AC Motors** – Run on AC supply
- 3 **Universal Motors** – Run on either AC or DC

Note: AC motors are more common because:

- Most supply systems are AC
- AC motors are **simpler and cheaper**

2.5.1 Back EMF in DC Motors

What is Back EMF?

- When motor runs, armature conductors **cut magnetic flux**
- This induces an emf (generator effect)
- Direction is **opposite** to applied voltage
- Called **counter or back emf (E_b)**

Key Points:

- $E_b \propto \text{speed (N) and flux } (\Phi)$
- **Same formula** as generator EMF:

$$E_b = (P \times \Phi \times Z \times N) / (60 \times b) = K_1 \times \Phi \times N$$

Armature Current:

$$I_a = (V - E_b) / R_a$$

2.5.2 Significance of Back EMF

Acts Like a Governor:

- **High speed** → E_b large → I_a small → less torque
- **Low speed** → E_b small → I_a large → more torque
- Motor is **self-regulating**

"Back EMF makes motor draw just enough current"

2.5.3 Voltage Equation of DC Motor

Fundamental Equation:

$$V = E_b + I_a \times R_a$$

What This Means: Applied voltage (V) overcomes:

- 1 Back EMF (E_b)
- 2 Armature resistance drop (I_aR_a)

Power Equation (multiply by I_a):

$$V \times I_a = E_b \times I_a + I_a^2 \times R_a$$

- $V I_a$ = Power supplied to armature
- $I_a^2 R_a$ = Copper loss (heat)
- $E_b I_a$ = Mechanical power developed

Example 4 – Generator vs Motor EMF

Problem: $R_a = 0.1\Omega$, $V = 250V$

(a) As Generator ($I_a = 80A$):

$$E_g = V + I_a R_a = 250 + (80 \times 0.1) = 258V$$

(b) As Motor ($I_a = 60A$):

$$E_g = V - I_a R_a = 250 - (60 \times 0.1) = 244V$$

Key Difference: Generator: $E_g = V + I_a R_a$ | Motor: $E_b = V - I_a R_a$

2.5.4 Power and Torque Equations

Power Relations:

$$\begin{aligned} \text{Input Power} &= V \times I_a \\ \text{Copper Loss} &= I_a^2 \times R_a \\ \text{Mechanical Power} &= E_b \times I_a \\ \text{Efficiency} &= E_b / V \text{ (approx.)} \end{aligned}$$

Torque Equation:

$$T_a = E_b \times I_a / (2\pi \times N)$$

After Substitution:

$$T_a = (1/2\pi) \times \Phi \times Z \times I_a \times (P/b)$$

Simplified:

$$T_a = K_2 \times \Phi \times I_a$$

Important: Torque is **independent of speed**!

Summary:

Generator	Motor
$E_g = K_1 \Phi N$	$T_a = K_2 \Phi I_a$
Voltage depends on speed	Torque depends on current

2.5.5 Speed of DC Motor

Speed Equation:

$$N = (V - I_a \times R_a) / (K_1 \times \Phi) = E_b / (K_1 \times \Phi)$$

Approximation:

$$N \approx V / (K_1 \times \Phi)$$

(Since armature drop is < 5% of V)

Key Concept: Speed is **inversely proportional** to flux

Example 5 – Speed Change with Voltage and Flux

Problem: Motor runs at 900 rpm on 460V. New voltage = 200V, new flux = 0.7 × original

$$\begin{aligned} N_2/N_1 &= (V_2/V_1) \times (\Phi_1/\Phi_2) \\ N_2 &= (200/460) \times (\Phi_1/0.7\Phi_1) \times 900 \\ N_2 &= 559 \text{ rpm} \end{aligned}$$

2.5.6 Shunt Motors**Connection:**

- Field winding in **parallel** with armature
- Field rheostat in series with field for speed control

Current Relations:

$$I = I_a + I_{sh} \text{ (Motor)}$$

(Compare to generator: $I_a = I + I_{sh}$)

Speed Characteristics

- **Practically constant speed**
- Speed drops **slightly** with load
- Classed as **constant-speed motor**

Speed Equation:

$$N = (V - I_a R_a) / (K_1 \Phi)$$

Torque Characteristics

Flux is **practically constant**

$$T_a \propto I_a$$

Torque increases **linearly** with current

Speed-Torque Characteristics

- Torque: Straight-line relationship with I_a
- Speed: Slight drop with load
- Armature reaction causes some speed increase (counteracts drop)

Applications

- **Constant speed drives**
- Machine tools
- Blowers and fans

- Lathes and woodworking machines
- Line shafts

Advantage: Safe when load is suddenly removed (no excessive speed)

2.5.7 Series Motors

Connection:

- Field winding in **series** with armature
- Same current flows through both

Current Relations:

$$I = I_a = I_{se}$$

(For both generator and motor)

Speed Characteristics

- Speed decreases **appreciably** with load
- Speed is **inversely proportional** to flux
- Stronger flux → lower speed

Speed Equation:

$$N = (V - I_a(R_a + R_{se})) / (K_1 \Phi)$$

Torque Characteristics

Before saturation: $\Phi \propto I_a$

$$T_a \propto I_a^2$$

Torque increases as **square of current**

Example: Double current → 4× torque!

Speed-Torque Characteristics

- **High starting torque**
- Torque $\propto I^2$ (before saturation)
- Large speed variation with load

Applications

- **High starting torque** situations
- **Hoists and cranes**
- **Traction** (electric trains)
- Electric locomotives
- Wide load variations

Advantage for Traction:

- Huge starting torque
- Speed automatically adjusts to load

2.5.8 Speed Control of DC Motors

Speed Regulation

Definition: Ability to maintain constant speed for varying loads

$$SR = [(No\text{-}load\ speed - Full\text{-}load\ speed) / Full\text{-}load\ speed] \times 100\%$$

Three Control Methods

Method	How It Works	Effect
1. Armature Resistance Control	Variable resistor in series with armature	Increases $R_a \rightarrow$ decreases speed
2. Field Flux Control	Field rheostat in series with field	Increases $R_f \rightarrow$ decreases flux $\rightarrow$ increases speed
3. Voltage Control	Power electronics (thyristors)	Vary applied voltage $\rightarrow$ vary speed

Field Control Principle

- **Increasing** field resistance $\rightarrow$ **lower** flux $\rightarrow$ **higher** speed
- **Decreasing** field resistance $\rightarrow$ **higher** flux $\rightarrow$ **lower** speed

Example 7 – Speed Calculation

Problem: 600V shunt motor, $R_a = 0.14\Omega$, No-load: $N=800$ rpm, $I_a=12$ A, Full-load: $I_a=225$ A

$$E_{nl} = 600 - (12 \times 0.14) = 598.32\text{ V}$$

$$E_{fl} = 600 - (225 \times 0.14) = 568.50\text{ V}$$

(a) Constant flux:

$$N_{fl} = (568.50/598.32) \times 800 = 760\text{ rpm}$$

(b) Flux reduced to 95%:

$$N = (568.50/598.32) \times (1/0.95) \times 800 = 800\text{ rpm}$$

(c) Flux reduced to 80%:

$$N = (568.50/598.32) \times (1/0.80) \times 800 = 950\text{ rpm}$$

SUMMARY TABLE: SHUNT vs SERIES MOTORS

Feature	Shunt Motor	Series Motor
Connection	Field parallel to armature	Field series with armature
Speed	Nearly constant	Varies greatly with load
Speed Equation	$N = E_b / (K_1 \Phi)$	$N = E_b / (K_1 \Phi)$ (with R_{se} added)
Torque	$T \propto I_a$ (linear)	$T \propto I_a^2$ (before saturation)
Starting Torque	Moderate	Very high
Applications	Constant speed drives	High starting torque (cranes, trains)
Unsafe condition	No-load (runaway)	Light load (high speed)

KEY EQUATIONS SUMMARY

Generator

Equation	Meaning
$E_g = PZN / (60b)$	Generated emf
$E_g = K_1 \Phi N$	Simplified form
$V = E_g - I_a R_a$	Terminal voltage (shunt)
$I_a = I + I_{sh}$	Current relation (shunt gen)
$V = E_g - I(R_a + R_{se})$	Terminal voltage (series gen)

Motor

Equation	Meaning
$E_b = PZN / (60b)$	Back emf
$V = E_b + I_a R_a$	Voltage equation
$T_a = K_2 \Phi I_a$	Torque equation
$N = (V - I_a R_a) / (K_1 \Phi)$	Speed equation
$\eta = E_b / V$	Efficiency (approx)